



UNIVERZITET U TUZLI
FAKULTET ELEKTROTEHNIKE



VHDL: uslovno i selektivno dodjeljivanje signala, case, enumeratori, konstante, konverzija toka podataka

Dr. Sc. Asmir Gogić, vanr. prof.

Tuzla, 2020.

Conditional Signal Assignment

- Dosada smo vidjeli da se konkurentni signali vežu za jedan izraz!
- VHDL omogućuje mehanizme uslovnog dodjeljivanja vrijednosti signala **Conditional Signal Assignment** po sljedećem principu

```
<target> <= <expression> when <condition> else
<expression> when <condition> else
<expression>;
```

- Princip sličan if else lancu gdje je evidentan prioritet tokom selektovanja izlaza.
- Za slučaj da imamo dva uslova da su zadovoljena, biti će izvršen prvi odozgo u implementaciji modela.

PRIMJER 1

Napisati VHDL kod koji će implementirati funkcionalnost digitalnog sklopa koji poredi dva dvo-bitna binarna broja. Izlaz digitalnog sklopa je 1 ako su binarni brojevi jednaki u suprotnom je u stanju 0.

Conditional Signal Assignment

- Ako pogledamo tablicu stanja logičkog sklopa...

Ulaz 1		Ulaz 0		Izlaz
A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

$$Y = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}C\overline{D} + ABCD$$

Conditional Signal Assignment

- Dosadašnja spoznaja o VHDL-u bi nam omogućila sljedeću implementaciju...

```
library ieee;
use ieee.std_logic_1164.all;
entity comp is
  port (
    -- dva dvo-bitna ulaza
    a , b : in std_logic_vector (1 downto 0);
    -- jednobitni izlaz
    y : out std_logic);
end comp;

architecture fun_arch of comp is
  -- pomocni signali
  signal p0,p1,p2,p3: std_logic;
begin
  -- izlaz je suma pomocnih signala
  y <= p0 or p1 or p2 or p3;
  -- pomocni signali kao potpuni proizvodi
  p0 <= ((not a(1)) and (not b(1))) and ((not a(0)) and (not b(0)));
  p1 <= ((not a(1)) and (not b(1))) and (a(0) and b(0));
  p2 <= (a(1) and b(1)) and ((not a(0)) and (not b(0)));
  p3 <= (a(1) and b(1)) and (a(0) and b(0) ) ;
end fun_arch;
```

Conditional Signal Assignment

- ... korištenjem uslovnog dodjeljivanja imamo sljedeću implementaciju...

```
library ieee;
use ieee.std_logic_1164.all;
entity comp is
    port (
        -- dva dvo-bitna ulaza
        a , b : in std_logic_vector (1 downto 0);
        -- jednobitni izlaz
        y : out std_logic);
end comp;

architecture fun_arch of comp is
begin
    y <= '1' when (a(1)='0' and b(1)='0' and a(0)='0' and b(0)='0') else
    '1' when (a(1)='0' and b(1)='1' and a(0)='0' and b(0)='1') else
    '1' when (a(1)='1' and b(1)='0' and a(0)='1' and b(0)='0') else
    '1' when (a(1)='1' and b(1)='1' and a(0)='1' and b(0)='1') else
    '0';
end fun_arch;
```

Selected Signal Assignment

- **Selected Signal Assignment** - predstavlja još jedan način dodjeljivanja vrijednosti signala gdje se dodjeljivanje izvodi samo ako se pojavi odabrani set signala

```
with <choose_expression> select  
    target <= <expression> when <choices>,  
    <expression> when <choices>;
```

- Princip sličaj case/when iskazima gdje prioritet u izvršavanju nije bitan.
- ... primjer multipleksera 4/1:

```
entity mux_4on1_entity is  
port(  
    D3,D2,D1,D0 : in std_logic;  
    SEL: in std_logic_vector(1 downto 0);  
    MX_OUT : out std_logic);  
end mux_4on1_entity;  
architecture mux_4on1_arch of mux_4on1_entity is  
begin  
    with SEL select  
        MX_OUT <= D3 when "11",  
                  D2 when "10",  
                  D1 when "01",  
                  D0 when "00",  
                  '0' when others;  
end mux_4on1_arch;
```

Case statement

- **Case** iskaz selektuje jedan od alternativnih sekvenci iskaza na bazi vrijednosti izraza.
- Za razliku od **if** iskaza, **test ne mora biti bool tip**, nego može biti signal, varijabla ili izraz.
- **Case** iskaz se koristi kada postoji veliki broj mogućih ishoda.
- Opšta sintaksa je:

```
case expression is
  when options_1 =>
    statement_sequence
    ...
  when options_n =>
    statement_sequence
  [when others =>
    statement_sequence]
end case;
```

- **Case** iskaz sadrži više **when** klauzula i svaka od njih može imati jedan ili više izraza. Ako je izraz vrijednost, iste se odvajaju sa | karakterom

Case statement

```
case expression is
  when val =>
    statement_sequence
  when val1 | val2 | ... | valn =>
    statement_sequence
  when val3 to val4 =>
    statement_sequence
  when val5 to val6 | val7 to val8 =>
    statement_sequence
  ...
  when others =>
    statement_sequence
end case;
```


VHDL - enumerators, constants

- Predstavlja korisnički definiran **tip podataka** sa **simboličkim vrijednostima**.
- U osnovi omogućuje zamjenu klasičnih decimalnih odnosno relanih vrijednosti sa simboličkim imenima.

```
type state_t is (INIT, WAIT4ACCESS, READ, ERASE, WRITE);
```

```
-- primjer
signal curr_state: state_t;
signal prev_state: state_t;
curr_state <= INIT;
```

- **Konstantama** za razliku od enumeratora mora eksplicitno **dodjeliti vrijednosti**.
- Osiguravaju isti koncept kao i enumeratori.
- Nedostatak konstanti je u činjenici da možemo imati dvije različite konstante koje koristimo u FSM a da imaju iste vrijednosti.
- ... kod enumeratora se to ne može desiti


```
constant <constant_name> : <type> := <value>;
```

```
-- primjer
constant BUSWIDTH : integer := 8;
signal datain: signed(BUSWIDTH-1 downto 0) := x"00";
```

VHDL - enumerators

PRIMJER 2

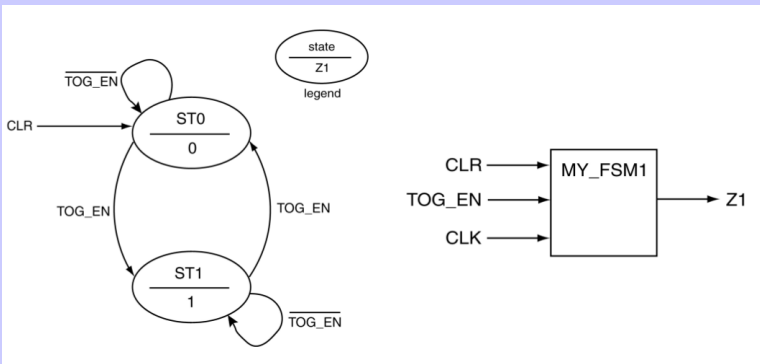Implementirati VHDL model FSM-a prikazanog na slici koristeći procese i enumeratore.



VHDL - enumerators

```

entity my_fsm1 is
  port ( TOG_EN : in std_logic;
        CLK,CLR : in std_logic;
        Z1 : out std_logic);
end my_fsm1;
architecture fsm1 of my_fsm1 is
  type state_type is (ST0,ST1); -- enumeratori
  signal PS,NS : state_type; -- PS - previous state, NS - new state

begin
  sync_proc: process(CLK,NS,CLR)
  begin
    -- take care of the asynchronous input
    if (CLR = '1') then
      PS <= ST0;
    elsif (rising_edge(CLK)) then
      PS <= NS;
    end if;
  end process sync_proc;

```

VHDL - enumerators

```
comb_proc: process(PS,TOG_EN)
begin
  Z1 <= '0'; -- pre-assign output
  case PS is
    when ST0 => -- items regarding state ST0
      Z1 <= '0'; -- Moore output
      if (TOG_EN = '1') then NS <= ST1;
      else NS <= ST0;
      end if;
    when ST1 => -- items regarding state ST1
      Z1 <= '1'; -- Moore output
      if (TOG_EN = '1') then NS <= ST0;
      else NS <= ST1;
      end if;
    when others => -- the catch-all condition
      Z1 <= '0'; -- arbitrary; it should never
      NS <= ST0; -- make it to these two statements
  end case;
end process comb_proc;
end fsm1;
```

PRIMJER 3

Implementirati **testbench** za prethodni primjer.

VHDL - enumerators

- Sljedeći primjer procesa koji mijenja vrijednost varijable *next_color* na bazi trenutne vrijednosti boje definirane u enumeratoru *type_color*.

```
type type_color is (red, yellow, green);  
process (color)  
  case color is  
    when red =>  
      next_color <= green;  
    when yellow =>  
      next_color <= red;  
    when green =>  
      next_color <= yellow;  
  end case;  
end process;
```

Konverzija toka podataka - zašto?

- Generalno postoje dva tipa prijenosa podataka: **serijski i paralelni**.
- **Serijski prijenos** podataka karakterizira sukcesivno emitovanje¹ simbola/bita kroz komunikacijski kanal (žičani ili bežični) prema nekom predefiniranom redoslijedu².
- Prijenos podataka u osnovnom opsegu žičanim medijem se odvija u blokovima od Nx8 bita pri čemu sa odgovarajućim **START** i **STOP** signalima naglašava početak i kraj prijenosa bloka podataka.
- Veliki broj serijskih protokola pored informacionih/start/stop bita/simbola emituju i zaštitne bite³
- **Paralelni prijenos** omogućuje simultani prijenos cijelog bloka podataka ili dijela bloka podataka.
- Najčešći broj paralelnih komunikacijski kanala (električnih vodova) je 2,4,8,16,32,64...
- Postoje i hibridne verzije serijsko-paralelnog prijenosa kao što je primjer kod QSPI i OCTA SPI protokola, USB3, MIPI DSI/CSI, HDMI, LVDS,...

¹jedan za drugim


²najznačajniji prema najmanje značajnom i obrnuto

³Koji su rezultat kanalnog kodiranja, npr bit pariteta kod U(S)ART-a, CRC kod SPI, itd

Konverzija toka podataka - primjer

PRIMJER 4

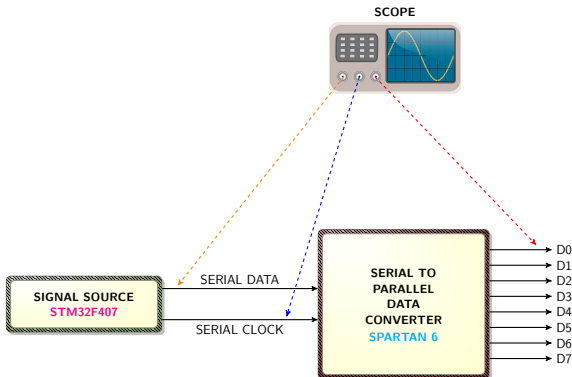Razviti VHDL model serijsko-paralelnog konvertora podataka koji ima dva ulaza SDATA i SCLK te jedan 8 bitni izlaz POUT. Signal SDATA predstavlja podatke a SCLK takt impulse nekog eksternog modula. Serijski podaci na ulazu SDATA dolaze u grupama od po 8 bita a vrijednost bita je validna na negativnoj ivici SCLK takt impulsa. Konvertor treba da nakon detekcije osmog bita postavi stanje izlaza POUT.




Srednja vrijednost diskretnog signala

- Proračun srednje vrijednost signala izvodimo sa tzv. **moving average** filter (MAF) koji u osnovi pronalazi aritmetičku sredinu predefiniranog seta uzoraka.
- Pogodan je za odstranjivanje viših harmonijskih komponenti, slučajnog šuma odnosno za ugačavanje signala.
- Impulsni odziv FIR MAF-a je

$$h[n] = \frac{1}{N} \sum_{k=0}^{N-1} \delta[n - k] \quad (1)$$

- MAF je ustvari LPF čija je granična frekvencija f_s/N .
- Koeficijenti filtera su isti i iznose $1/N$.


Srednja vrijednost diskretnog signala

 


Srednja vrijednost diskretnog signala

PRIMJER 8

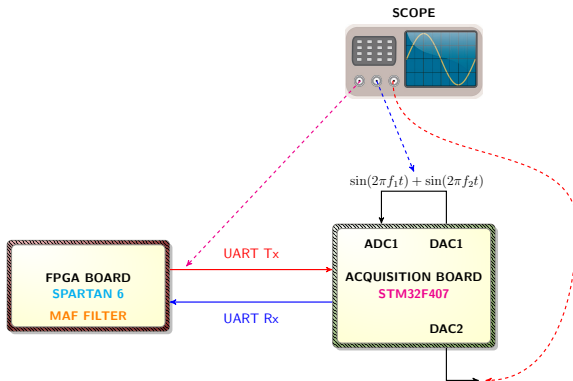
Razviti VHDL model MAF digitalnog filtera N koeficijenta. Ulaz MAF-a predstavljaju uzorci ADC-a čija je frekvencija uzorkovanja 10 kHz a signal poruke je $\sin(200\pi t) + \sin(1000\pi t)$. Razmjena podataka između ADC-a i FPGA čipa izvodi se UART serijskim protokolom čiji je baudrate 921600 bauda.. Analizirati utjecaj reda filtera na graničnu frekvenciju filtera.




MAF - Matlab rezultati N=2

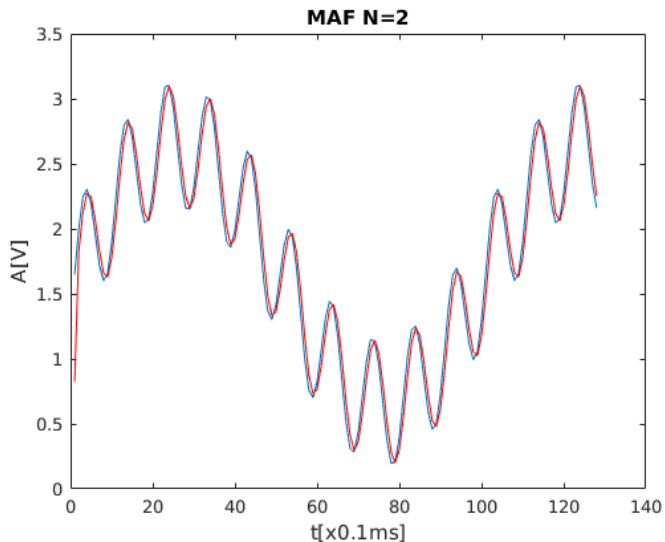

MAF - Matlab rezultati N=8

 

MAF - Matlab rezultati N=32

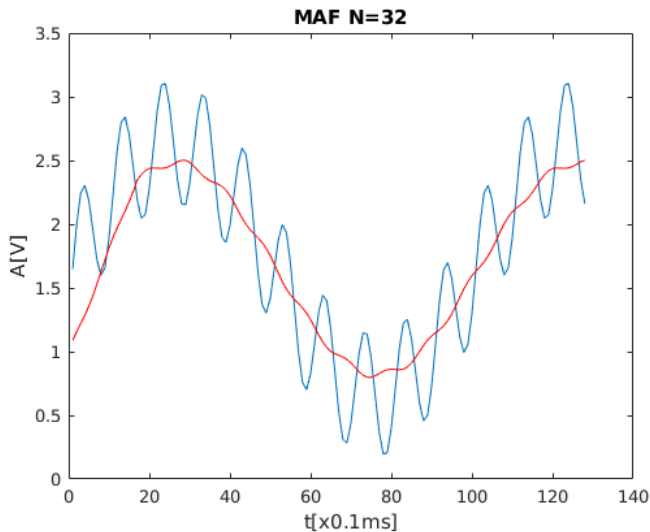

P-I
ooooo


P-II
oo

P-III
ooooo

P-IV
oooooooo●ooooo

P-V
o

MAF - FPGA rezultati N=2

 

P-I
ooooo


P-II
oo

P-III
ooooo

P-IV
oooooooooooo●ooooo

P-V
o

MAF - FPGA rezultati N=8

 

P-I
ooooo


P-II
oo

P-III
ooooo

P-IV
oooooooooooo●oooo

P-V
o

MAF - FPGA rezultati N=32

 

P-I
ooooo


P-II
oo

P-III
ooooo

P-IV
oooooooooooo●ooo

P-V
o

MAF - FPGA rezultati N=64

 

VHDL resize & conversion

From type	To type	Conversion function
std_logic_vector	unsigned	unsigned(arg)
std_logic_vector	signed	signed(arg)
unsigned	std_logic_vector	std_logic_vector(arg)
signed	std_logic_vector	std_logic_vector(arg)
integer	unsigned	to_unsigned(arg, size)
integer	signed	to_signed(arg, size)
unsigned	integer	to_integer(arg)
signed	integer	to_integer(arg)
integer	std_logic_vector	integer -> unsigned/signed -> std_logic_vector
std_logic_vector	integer	std_logic_vector -> unsigned/signed -> integer
unsigned + unsigned	std_logic_vector	std_logic_vector(arg1 + arg2)
signed + signed	std_logic_vector	std_logic_vector(arg1 + arg2)
Type	Resize function	
unsigned	resize(arg, size)	
signed	resize(arg, size)	

P-I
ooooo


P-II
oo

P-III
ooooo

P-IV
ooooooooooooooooo●o

P-V
o

MAF - overflow issue!

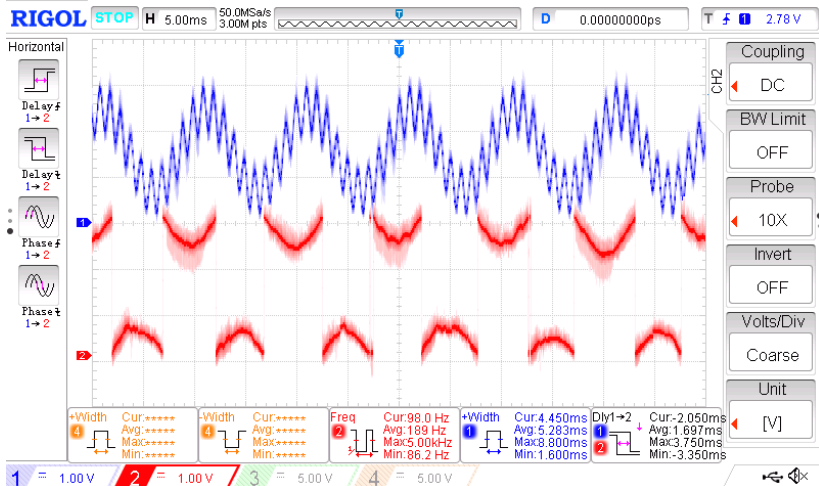

FPGA DEV Board

FPGA BASE BOARD

FPGA: **Spartan VI XC6SLX9**
MEMORY: **SST25VF032B**
PROGRAMMER: **STM32F103 MCU**
ADC: **3x channels via MCU**
UART: **1x via MCU**
LEDs: **8x**
SWITCHs: **2x**

TELECOMMUNICATION SHIELD1

MCU: **STM32F303CBT6**
DAC: **2ch 12bit@1Msps via MCU**
ADC: **10ch 12bit@5Msps via MCU**
DSS: **15MHz bandwidth**
ADAC: **32bit/384kHz PCM5101**
DMIC: **61dB/-26dB MP45DT02**
DISP: **84x48 monochrome N5100**
SWITCHs: **4x**

2x80 IO Headers

TELECOMMUNICATION SHIELD2

SMLED1: **WS2812**
SMLED2: **APA102C**
SMLED3: **TLC59731**
ADC: **860-SPS, 16Bit ADS1115**
EEPROM: **AT24C16**
RTC: **DS1302**
BUZZER: **1x 2.7kHz**
TMP SENSOR: **LM75**
DISP: **84x48 monochrome N5100**
SWITCHs: **4x**

2x80 IO Headers

Literatura

- RTL Hardware Design Using VHDL: Coding for Efficiency, Portability, and Scalability, 1st Edition by Pong P. Chu, 2006.
- Digital Systems Design Using VHDL 2 nd Edition, by Charles H. Roth, Jr. and Lizy Hurian John, Thomson, 2007.
- The Designer's Guide to VHDL, Third Edition, Peter J. Ashenden, 2008.